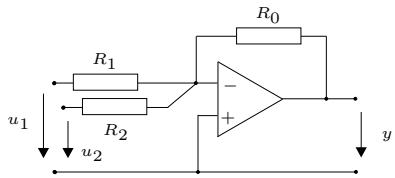
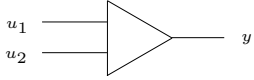
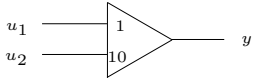
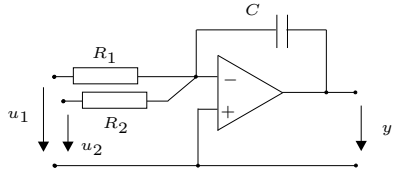
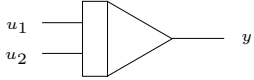
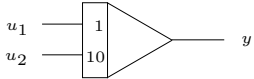
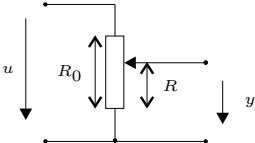


Schaltung	Komponenten	I/O-Gleichung	Symbol Analogrechner
 Summator mit Vorzeichenwechsel	$R_0 = R_1 = R_2 = 1 \text{ [M}\Omega\text{]}$ $K = \frac{R_0}{R_1} = \frac{R_0}{R_2} = 1$	$y(t) = -K[u_1(t) + u_2(t)]$ $= -u_1(t) - u_2(t)$	
	$R_0 = R_1 = 1 \text{ [M}\Omega\text{]}$ $R_2 = R_1/10$ $K_1 = \frac{R_0}{R_1} = 1 \quad K_2 = \frac{R_0}{R_2} = 10$	$y(t) = -K_1 u_1(t) - K_2 u_2(t)$ $= -u_1(t) - 10 \cdot u_2(t)$	
 Integrator mit Vorzeichenwechsel	$C = 1 \text{ [}\mu\text{F}\text{]}$ $R_1 = R_2 = 1 \text{ [M}\Omega\text{]}$ $K = \frac{1}{R_1 C} = \frac{1}{R_2 C} = 1 \text{ [s}^{-1}\text{]}$	$\frac{dy(t)}{dt} = -K[u_1(t) + u_2(t)]$ $= -u_1(t) - u_2(t)$	
	$C = 1 \text{ [}\mu\text{F}\text{]}$ $R_1 = 1 \text{ [M}\Omega\text{]} \quad R_2 = R_1/10$ $K_1 = \frac{1}{R_1 C} = 1 \text{ [s}^{-1}\text{]} \quad K_2 = 10 \text{ [s}^{-1}\text{]}$	$\frac{dy(t)}{dt} = -K_1 u_1(t) - K_2 u_2(t)$ $= -u_1(t) - 10 \cdot u_2(t)$	
 Spannungsteiler (passiv)	$R_0 = 1 \text{ [M}\Omega\text{]}$ $K = \frac{R}{R_0} \in [0 \dots 1]$	$y = K \cdot u(t)$	